

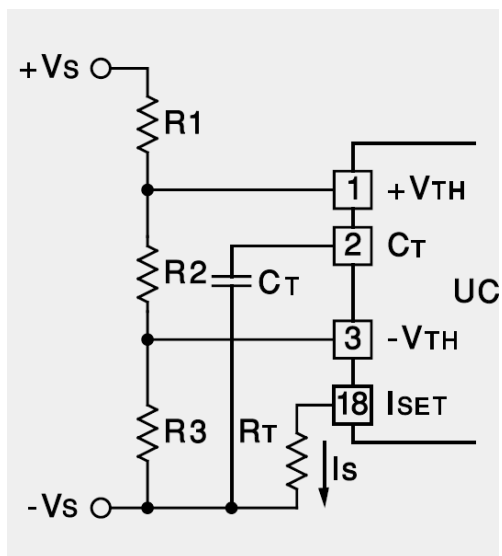


# SWITCHED MODE CONTROLLER FOR DC MOTOR DRIVE

UC1637 UC2637 UC3637

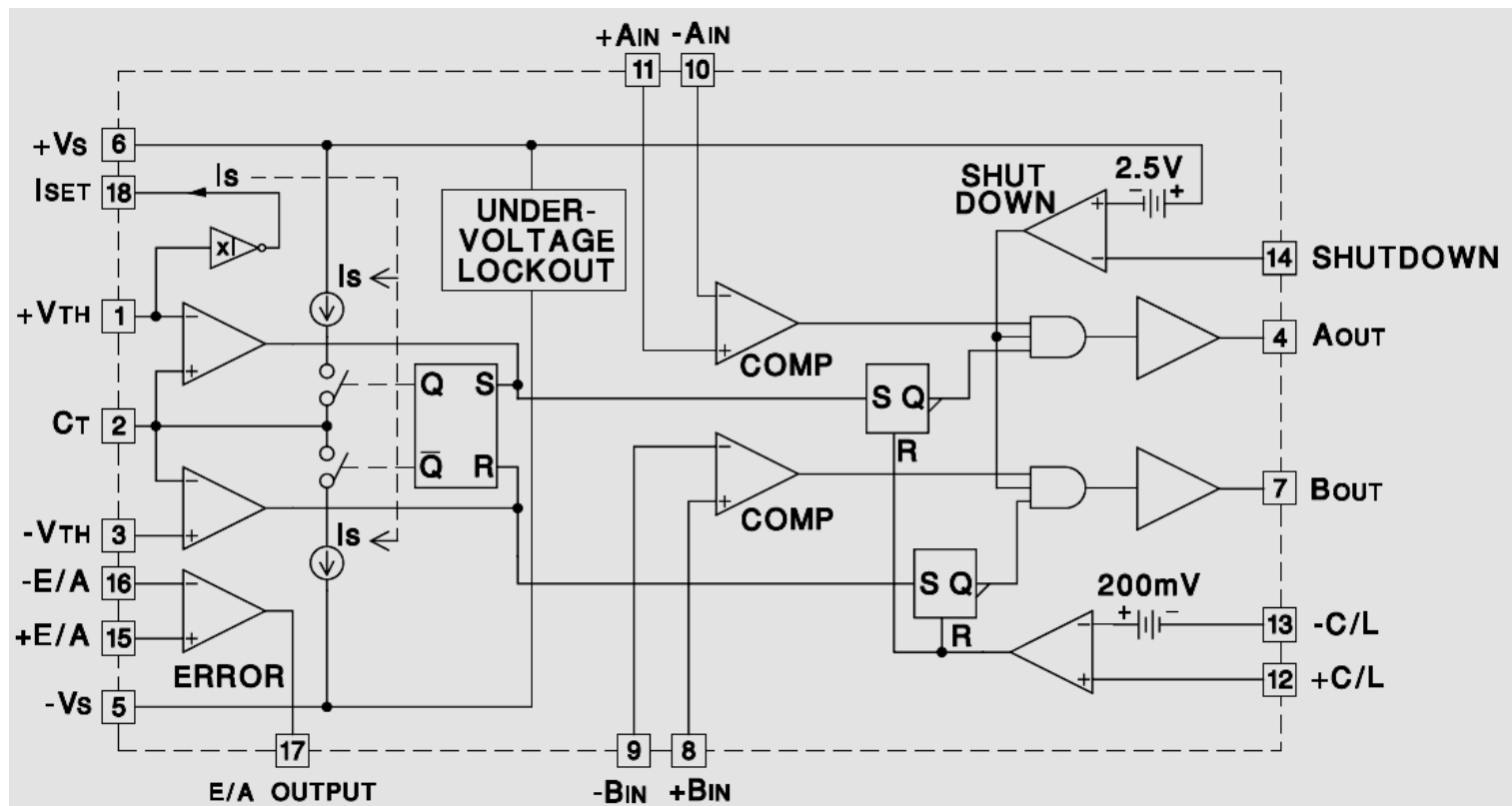

Generator sygnału trójkątnego

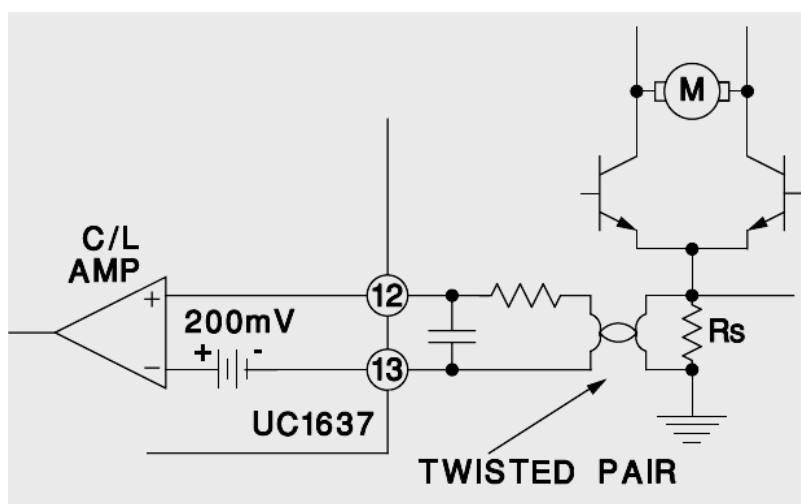

Zabezpieczenie prądowe

## Modulator PWM

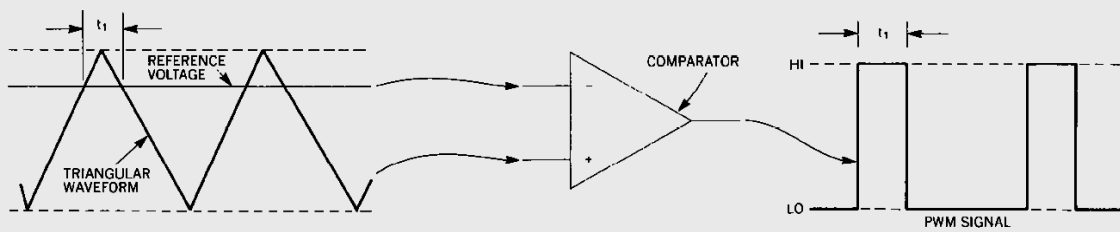
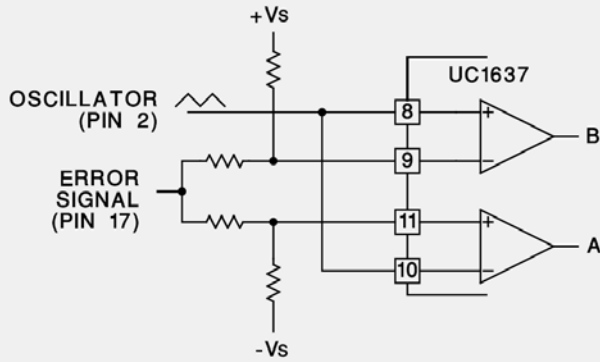


FIGURE 2. HOW A PWM SIGNAL IS GENERATED.



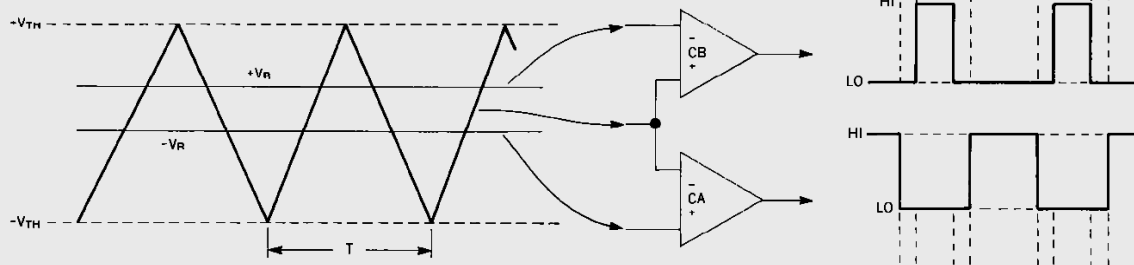
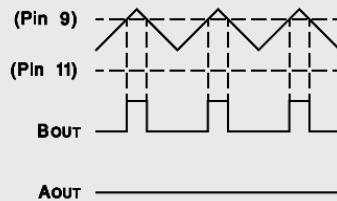
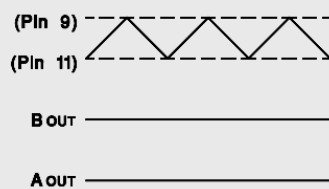


FIGURE 3. TWO PWM SIGNALS ARE GENERATED IN THE UC1637.

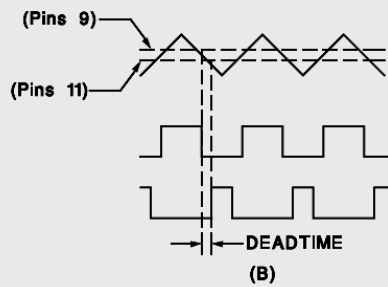

(C)

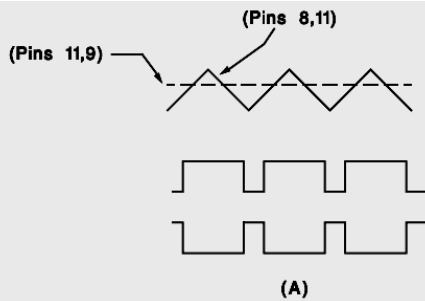